

UNIVERSITY OF GREATER MANCHESTER

**SCHOOL OF ENGINEERING AND BUILT
ENVIRONMENT**

**BENG (HONS) ELECTRICAL & ELECTRONIC
ENGINEERING**

SEMESTER ONE EXAMINATIONS 2025/2026

**INTERMEDIATE ELECTRICAL PRINCIPLES &
ENABLING POWER ELECTRONICS**

MODULE NO: EEE5013

Date: Wednesday 14th January 2026

Time: 10am – 12:30pm

INSTRUCTIONS TO CANDIDATES:

There are Five questions.

Answer **ANY FOUR** questions.

All questions carry equal marks.

Marks for parts of questions are shown in brackets.

Electronic calculators may be used provided that data and program storage memory is cleared prior to the examination.

CANDIDATES REQUIRE:

Formula Sheet (attached).

Question 1

- a) Sketch an equivalent circuit of an ideal operational amplifier.

[7 marks]

- b) Using Figure Q1, derive an expression for the output V_o of the following circuit in terms of the input voltages V_1 and V_2 .

[14 marks]

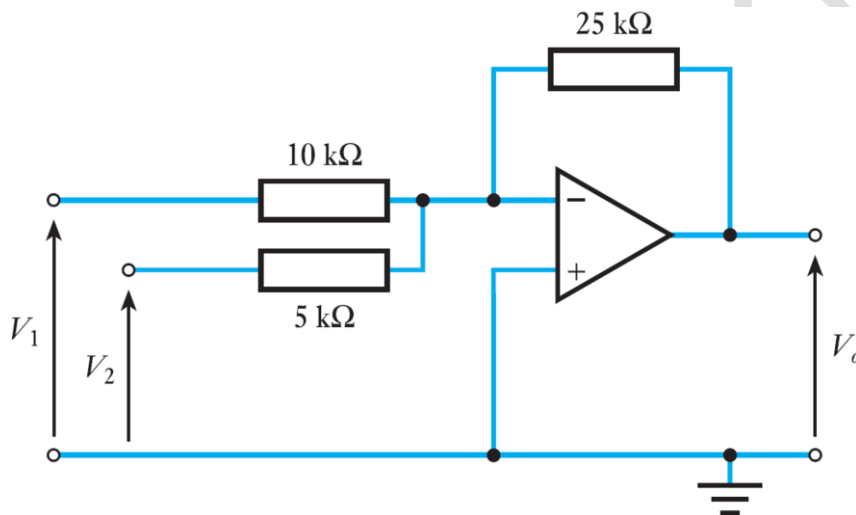


Figure Q1

- c) Also, determine the output voltage if $V_1 = 1$ V and $V_2 = 0.5$ V.

[4 marks]

[Total 25 marks]

PLEASE TURN THE PAGE

Question 2

- a) State three methods of cooling and explain each one briefly.

[6 marks]

- b) Consider a laptop CPU operated without a heatsink. The thermal resistance from Junction-Ambient is $58^{\circ}\text{C}/\text{W}$ and maximum junction temperature is 98°C with junction to case thermal resistance of $8^{\circ}\text{C}/\text{W}$, assuming a room temperature of 25°C .

- i. Determine the maximum power dissipated.
- ii. the power derating factor.

[4 marks]

- c) Assume the CPU in part (b) operated with a heatsink. The thermal resistivity of the heatsink is $188.58 \times 10^{-2} \text{ }^{\circ}\text{Cm}/\text{W}$, thickness is $3.22 \times 10^{-6} \text{ m}$ and contact area is $44.78 \times 10^{-6} \text{ m}^2$. Determine, the thermal resistance from sink-to-ambient.

[5 marks]

- d) A pipe of 20mm diameter is carrying 0.3 kg/s of water the flow then passes into a pipe of 10mm diameter if the density of water is $1000\text{kg}/\text{m}^3$.

- i. Calculate the volumetric flow rate and the average velocity of the water in the 20 mm pipe.
- ii. Calculate the average velocity of the water in the 10 mm pipe.

[10 marks]

[Total 25 marks]

PLEASE TURN THE PAGE

Question 3

Explain with the aids of diagrams the operation of a single-phase half-wave rectifier with inductive load.

[10 marks]

(a) A half-wave single-phase rectifier circuit is shown in figure Q3 below. The following are given:

$V_s=220$ V, $f=50$ Hz, diode forward voltage drop is assumed to be zero. Determine:

i. The load mean voltage and current for resistive load of 8 Ohms **[4 marks]**

ii. The load current ac component and shape for
 1. A pure resistive load of 8 Ω resistor and **[7 marks]**

2. An inductive load of 0.1 H inductance in series with the 8 Ω resistor **[4 marks]**

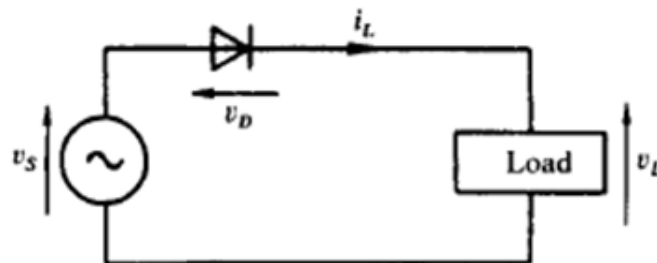


Fig. Q3 A single-phase half-wave rectifier circuit

[Total 25 marks]**PLEASE TURN THE PAGE**

Question 4

- (a) Draw a circuit diagram for a buck converter and derive an expression for $\frac{V_{out}}{V_{in}}$ defining all parameters used in this circuit.

[15 marks]

- (b) Enumerate the basic grounding system then explain what is meant by static grounding.

[10 marks]**[Total 25 marks]****Question 5**

- (a) Calculate the line voltages and the line currents of a Y-Y source-load Connection. Given: $V_{an} = 120 \angle 60^\circ \text{ V}$. The system is balanced three-phase system. The system impedances per phase are given as follows:

$$Z_{source} = 0.4 + j0.3 \Omega, Z_{line} = 0.6 + j0.7 \Omega, Z_{load} = 24 + j19 \Omega.$$

[12 Marks]

- b) Assume a delta-connected load, with each leg $Z = 100 \angle 80^\circ \Omega$, is supplied from a 3-phase supply with voltage of 13.8 kV (L-L) source. Find:

- i. The complex power of the source and load.

[6 marks]

- ii. The power factor at the load and the value of a shunt capacitor that brings the power factor to unity.

[3 marks]

- iii. The value of a shunt capacitor that brings the power factor of the load to unity. Assume system frequency is 50 Hz.

[4 marks]**[Total 25 marks]****END OF QUESTIONS****PLEASE TURN THE PAGE FOR FORMULA SHEET**

Formula sheet

These equations are given to save short-term memorisation of details of derived equations and are given without any explanation or definition of symbols; the student is expected to know the meanings and usage.

Converters:

$$\begin{aligned} \%THD_i &= 100 \times \frac{I_{dis}}{I_{s1}} \\ &= 100 \times \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} \\ &= 100 \times \sqrt{\sum_{h \neq 1} \left(\frac{I_{sh}}{I_{s1}}\right)^2} \end{aligned}$$

$$PF = \frac{V_s I_{s1} \cos \phi_1}{V_s I_s} = \frac{I_{s1}}{I_s} \cos \phi_1$$

$$DPF = \cos \phi_1$$

$$PF = \frac{I_{s1}}{I_s} DPF$$

$$PF = \frac{1}{\sqrt{1 + THD_i^2}} DPF$$

$$A_u = \sqrt{2} V_s (1 - \cos u) = \omega L_s I_d$$

$$\cos u = 1 - \frac{\omega L_s I_d}{\sqrt{2} V_s}$$

$$V_d = 0.45 V_s - \frac{\text{area } A_u}{2\pi} = 0.45 V_s - \frac{\omega L_s}{2\pi} I_d$$

$$V_d = 1.35 V_{LL} \cos \alpha - 3 \frac{\omega L_s}{\pi} I_d$$

$$\cos(\alpha + u) = \cos \alpha - 2 \frac{\omega L_s}{\sqrt{2} V_{LL}} I_d$$

$$\gamma = 180 - (\alpha + u)$$

$$V_L = \left[\frac{1}{T} \int_0^T v_L^2(t) dt \right]^{1/2}$$

$$V_{dc} = \frac{1}{T} \int_0^T v_L(t) dt$$

$$TUF = \frac{P_{dc}}{V_s I_s} = \frac{V_{dc} I_{dc}}{V_s I_s}$$

$$RF = \frac{V_{ac}}{V_{dc}}$$

$$(V_{peak} - V_{min}) = \frac{2P\Delta t}{(V_{peak} + V_{min})C}$$

$$\frac{di_L}{dt} = \frac{V_{in} - V_{out}}{L}$$

$$\sigma = \frac{P_{dc}}{P_L} = \frac{V_{dc} I_{dc}}{V_L I_L}$$

$$FF = \frac{V_L}{V_{dc}} \quad \text{or} \quad \frac{I_L}{I_{dc}}$$

PLEASE TURN THE PAGE

School of Engineering and Built Environment
 BEng (Hons) Electrical & Electronics Engineering
 Semester One Examination 2025/2026
 Intermediate Electrical Principles & Enabling Power Electronics
 Module No. EEE5013


$$V_{dca} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_{max} \sin(\omega t) d(\omega t) = \frac{V_{max}}{2\pi} (1 + \cos \alpha)$$

$$V_{ph} = \frac{V}{\sqrt{3}}, I_{ph} = I \text{ for star connection, } V_{ph} = V, I_{ph} = \frac{I}{\sqrt{3}} \text{ for delta connection}$$


$$S = \sqrt{3}VI \text{ V.A.}, P = \sqrt{3}VI \cos \theta \text{ W.}, Q = \sqrt{3}VI \sin \theta \text{ V.A.r}$$

$$Q_C = \sqrt{3}VI_C \text{ V.A.r.}, X_C = \frac{V}{\sqrt{3}I_C} \Omega$$

Three-phase systems

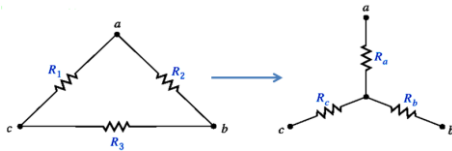

Delta to Star conversion:

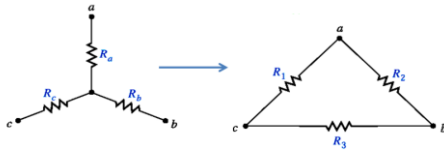

Star to Delta conversion:

Gravity:

$$9.81 \text{ m/s}$$

Thermal resistance of the interface material:

$$\theta_{cs} = \frac{(\rho)(t)}{A}$$

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

PLEASE TURN THE PAGE

Output voltage of a
 differentiator circuit:

$$v_0 = -R_2 C_1 \frac{dv_I}{dt}$$

Compressibility relationship:

$$K = -V \frac{dP}{dV}$$

General manometer:

$$\Delta P = | \Delta \rho g \Delta h |$$

Venturi meter:

$$v_{in} = C_D \sqrt{\frac{2 \Delta P}{\rho_f \left[\left(\frac{d_{large}}{d_{small}} \right)^4 - 1 \right]}}$$

Force on a submerged wall:

$$F = \frac{\rho g a h^2}{2}$$

Drag coefficient:

$$C_{Drag} = \frac{F_D}{\frac{1}{2} \rho v^2 A}$$

Flow through a small hole:

$$Q = C_D \sqrt{\frac{2 \Delta P}{\rho}} A$$

Flow through a rectangular slit:

$$Q = \frac{2}{3} C_D W \sqrt{2g} \left[(H_0 + L)^{\frac{3}{2}} - H_0^{\frac{3}{2}} \right]$$

Tank draining:

$$h^{\frac{1}{2}} = h_0^{\frac{1}{2}} - \frac{C_D a \sqrt{2g}}{2A} t$$

PLEASE TURN THE PAGE

School of Engineering and Built Environment
BEng (Hons) Electrical & Electronics Engineering
Semester One Examination 2025/2026
Intermediate Electrical Principles & Enabling Power Electronics
Module No. EEE5013

Flow over a rectangular weir:

$$Q = \frac{2}{3} C_D W \sqrt{2g} H^{\frac{3}{2}}$$

Flow over a V-notch weir:

$$Q = \frac{8}{15} C_D \tan\left(\frac{\theta}{2}\right) (2g)^{\frac{1}{2}} H^{\frac{5}{2}}$$

Poiseuille's Law:

$$Q = -\frac{\pi}{128\mu} \frac{dP}{dx} D^4$$

Darcy's Law:

$$\Delta P = \frac{2f L \rho \bar{u}^2}{D}$$

PLEASE TURN THE PAGE

Summary of phase and line voltages/currents for balanced three-phase systems.¹

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ Same as line currents	$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{V}_{an} / \mathbf{Z}_Y$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Y- Δ	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{AB} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{BC} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{CA} / \mathbf{Z}_\Delta$	$\mathbf{V}_{ab} = \mathbf{V}_{AB} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{BC} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{CA} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ - Δ	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{ab} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{bc} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{ca} / \mathbf{Z}_\Delta$	Same as phase voltages $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Δ -Y	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ Same as line currents	Same as phase voltages $\mathbf{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3}\mathbf{Z}_Y}$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$

END OF PAPER